

实验六 CPU 综合设计

一、实验目的

- 1 掌握复杂系统设计方法。
- 2 深刻理解计算机系统硬件原理。

二、实验内容

- 1) 设计一个基于 MIPS 指令集的 CPU，支持以下指令：{add, sub, addi, lw, sw, beq, j, nop};
- 2) CPU 需要包含寄存器组、RAM 模块、ALU 模块、指令译码模块;
- 3) 该 CPU 能运行基本的汇编指令; (D~C+)

以下为可选内容:

- 4) 实现多周期 CPU (B~B+);
- 5) 实现以下高级功能之一 (A~A+):
 - (1) 实现 5 级流水线 CPU;
 - (2) 实现超标量;
 - (3) 实现 4 路组相联缓存;

可基于 RISC V 、 ARM 指令集实现。

如发现代码为抄袭代码，成绩一律按不及格处理。

三、实验要求

编写相应测试程序，完成所有指令测试。

四、实验代码及结果

根据《Digital Design and Computer Architecture》书中的对 MIPS 流水线介绍与原理图加以改进，本实验实现了五级流水线的 CPU。

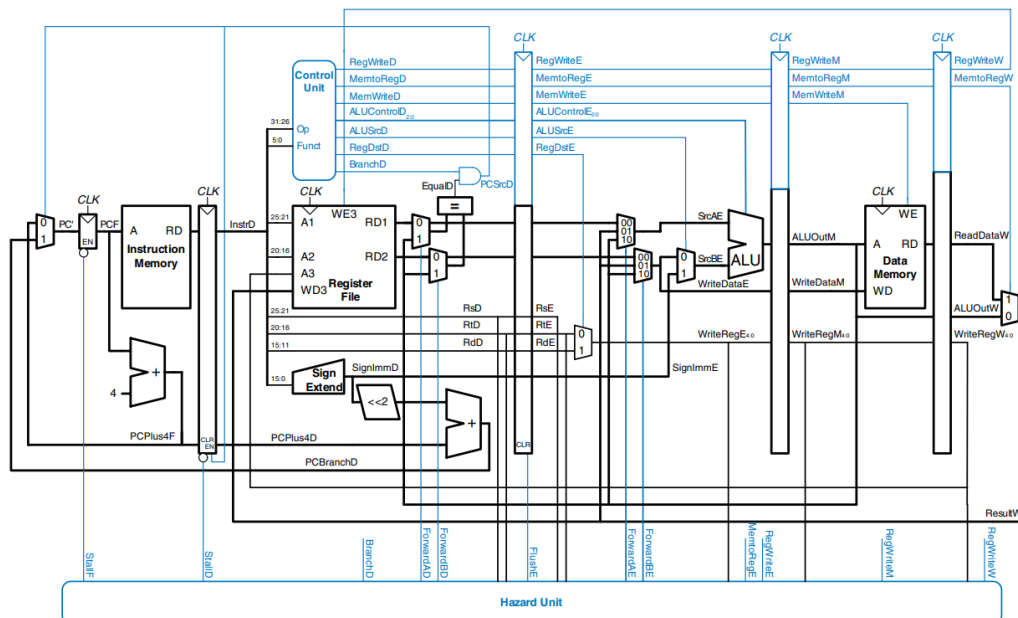


Figure 7.58 Pipelined processor with full hazard handling

- ▼ ● PipelineMIPSCPU (PipelineMIPSCPU.v) (12)
 - PC_1 : PCreg (PC.v)
 - L1I_cache : IMem (IMem.v)
 - IF_IDreg : IF_ID (IF_ID.v)
 - Register_1 : RegFile (RegFile.v)
 - > ● ctrl : Controller (Controller.v) (2)
 - ID_EXreg : ID_EX (ID_EX.v)
 - alu_forward_1 : ALU_Forward (ALU_Forward.v)
 - > ● alu : ALU_8 (ALU_8.v) (9)
 - EX_MEMreg : EX_MEM (EX_MEM.v)
 - > ● Dmem_1 : RAM_4Kx32_inout (RAM_4Kx32_inout.v) (9)
 - MEM_WBreg : MEM_WB (MEM_WB.v)
 - HZ : Hazard_unit (Hazard_Unit.v)

实验代码如下：

```

module PipelineMIPSCPU;
reg clk,rst;

wire [31:0] instruction;

wire CF,SF,PF,OF,Zero;

wire [5:0] opcode;
wire [4:0] rs, rt, rd;
wire [5:0] Funct;
wire [31:0] Data;
wire [31:0] PCF,PC_in,pcp4F,PCbranchD;

wire [31:0] ResultW;
wire stallF,stallD,flushE;
wire [1:0] forwardAE,forwardBE,forwardAD,forwardBD;

```

```

wire [31:0] SrcA,SrcB;
wire [31:0] pcp4D,IR;

wire RegWriteD, MemtoRegD, MemWriteD, ALUSrcD, RegDstD, BranchD,JumpD;
wire EqualD,PCSrcD;
wire [2:0] ALUControlD;
wire [31:0] Imm_extend;

wire RegWriteE, MemtoRegE, MemWriteE, ALUSrcE, RegDstE;
wire [2:0] ALUControlE;
wire [31:0] RD1E,RD2E,ImmE;
wire [4:0] rsE,rtE,rdE;

wire [31:0] SrcAE,SrcBE,alu_result,WriteDataE;

wire [4:0] WriteRegM,WriteRegE;
wire [31:0] ALUOutM,WriteDataM;
wire RegWriteM,MemtoRegM,MemWriteM;

wire [31:0] ReadDataW,ALUOutW;
wire [4:0] WriteRegW;
wire MemtoRegW,RegWriteW;
initial begin
    clk=0; rst=0;
end
always #10 clk=~clk;

assign PC_in=PCSrcD?PCbranchD:pcp4F;
PCreg PC_1(
    .clk(clk),
    .rst(rst),
    .pc(PCF),
    .pc_in(PC_in),
    .stall(stallF)
);
assign pcp4F=PCF+4;
assign PCbranchD=JumpD?IR[25:0]:(Imm_extend<<2)+pcp4D;
IMem L1I_cache(
    .A(PCF>>2),
    .RD(instruction)
);

```

```

IF_ID IF_IDreg(
    .clk(clk),
    .rst(rst),
    .In_pc(pcp4F),
    .In_Ins(instruction),
    .stall(stallD),
    .clr(PCSrcD),
    .out_pc(pcp4D),
    .out_Ins(IR)
);

assign    opcode = IR[31:26];
assign    rs = IR[25:21];
assign    rt = IR[20:16];
assign    rd = IR[15:11];
assign    Funct = IR[5:0];

```

```

RegFile Register_1(
    .CLK(clk),
    .WE3(RegWriteW),
    .RA1(rs),
    .RA2(rt),
    .WA3(WriteRegW),
    .WD3(ResultW),
    .RD1(SrcA),
    .RD2(SrcB),
    .RST(rst)
);

```

```

/*Control_Unit ctrl (
    .op(opcode),
    .funct(Funct),
    .RegWriteD(RegWriteD),
    .MemtoRegD(MemtoRegD),
    .MemWriteD(MemWriteD),
    .AluSrcD(ALUSrcD),
    .RegDstD(RegDstD),
    .BranchD(BranchD),
    .ALUControlD(ALUControlD)

```

```

);*/
Controller ctrl (
    .Op(opcode),
    .Funct(Funct),
    .RegWrite(RegWriteD),
    .MemToReg(MemtoRegD),
    .MemWrite(MemWriteD),
    .ALUSrc(ALUSrcD),
    .RegDst(RegDstD),
    .Branch(BranchD),
    .Jump(JumpD),
    .ALUControl(ALUControlD)
);

assign EqualD=( ( forwardAD==(2'b10)?ResultW:(forwardAD==(2'b01)?ALUOutM:SrcA))
    ==
    ( forwardBD==(2'b10)?ResultW:(forwardBD==(2'b01)?ALUOutM:SrcB)) );
assign PCSrcD=((BranchD|JumpD)&EqualD);
assign Imm_extend={ 16{IR[15]}},IR[15:0] };
ID_EX ID_EXreg(
    .clk(clk),
    .clr(flushE),

    .RD1((RegWriteW&&rs==WriteRegW)?ResultW:SrcA),
    .RD2((RegWriteW&&rt==WriteRegW)?ResultW:SrcB),
    .ImmD(Imm_extend),
    .rsD(rs),
    .rtD(rt),
    .rdD(rd),
    .RegWriteD(RegWriteD), .MemtoRegD(MemtoRegD), .MemWriteD(MemWriteD),
    .ALUSrcD(ALUSrcD), .RegDstD(RegDstD),
    .ALUControlD(ALUControlD),

    .rsE(rsE),.rtE(rtE),.rdE(rdE),
    .RD1E(RD1E),.RD2E(RD2E),.ImmE(ImmE),
    .RegWriteE(RegWriteE), .MemtoRegE(MemtoRegE), .MemWriteE(MemWriteE),
    .ALUSrcE(ALUSrcE), .RegDstE(RegDstE),
    .ALUControlE(ALUControlE)
);

```

//The ALUSrc here is used to control the sign-extend immediate expansion component,
//which means that for all non I-type instructions, immediate expansion is not required.

//At this point, the value of this component (ALUsrc) is 0, and for I-type instructions, its value is

1

```
ALU_Forward alu_forward_1(
    .forwardAE(forwardAE), .forwardBE(forwardBE),
    .ALUSrcE(ALUSrcE),
    .ALUOutM(ALUOutM), .ResultW(ResultW),
    .RD1E(RD1E), .RD2E(RD2E), .SignImmE(ImmE),

    .SrcAE(SrcAE), .SrcBE(SrcBE), .WriteDataE(WriteDataE)
);
```

```
ALU_8 alu (
    .A(SrcAE),
    .B(SrcBE),
    .OP(ALUControlE),
    .F(alu_result),
    .ZF(Zero),
    .CF(CF),
    .SF(SF),
    .PF(PF),
    .OF(OF)
);
```

```
assign WriteRegE=RegDstE?rdE:rtE;
```

```
EX_MEM EX_MEMreg(
    .alu_output(alu_result), .WriteDataE(WriteDataE),
    .WriteRegE(WriteRegE),
    .clk(clk), .rst(rst),
    .RegWriteE(RegWriteE), .MemtoRegE(MemtoRegE), .MemWriteE(MemWriteE),

    .ALUOutM(ALUOutM), .WriteDataM(WriteDataM),
    .WriteRegM(WriteRegM),
    .RegWriteM(RegWriteM), .MemtoRegM(MemtoRegM), .MemWriteM(MemWriteM)
);
```

```
Dmemory Dmem_1 (
    .Addr(ALUOutM),
    .Data_in(WriteDataM),
    .R_W(MemWriteM),
    .Data_out(Data),
```

```
.clk(clk)
```

```
);
```

```
MEM_WB MEM_WBreg(
```

```
.ALUOutM(ALUOutM), .ReadDataM(MemWriteM?32'b0:Data),
```

```
.clk(clk), .rst(rst),
```

```
.WriteRegM(WriteRegM),
```

```
.RegWriteM(RegWriteM), .MemtoRegM(MemtoRegM),
```

```
.ReadDataW(ReadDataW), .ALUOutW(ALUOutW),
```

```
.WriteRegW(WriteRegW),
```

```
.RegWriteW(RegWriteW), .MemtoRegW(MemtoRegW)
```

```
);
```

```
assign ResultW=MemtoRegW?ReadDataW:ALUOutW;
```

```
Hazard_unit HZ(
```

```
.rsD(rs), .rtD(rt),
```

```
.rsE(rsE), .rtE(rtE),
```

```
.BranchD(BranchD|JumpD),
```

```
.MemtoRegE(MemtoRegE), .RegWriteE(RegWriteE),
```

```
.MemtoRegM(MemtoRegM), .RegWriteM(RegWriteM),
```

```
.RegWriteW(RegWriteW),
```

```
.WriteRegE(WriteRegE), .WriteRegM(WriteRegM), .WriteRegW(WriteRegW),
```

```
.stallF(stallF), .stallD(stallD),
```

```
.forwardAD(forwardAD), .forwardBD(forwardBD), .flushE(flushE),
```

```
.forwardAE(forwardAE), .forwardBE(forwardBE)
```

```
);
```

```
endmodule
```

各模块代码:

```
module PCreg(  
    input wire clk,rst,  
    input wire[31:0] pc_in,  
    input wire stall,  
    output reg[31:0] pc  
);  
    initial begin  
        pc = 32'b0;  
    end  
    always@(posedge clk)begin  
        if(stall==1'b0)  
            pc <= pc_in;  
        else  
            pc <= pc;  
        end  
    endmodule
```

```
`define DATA_WIDTH 32  
module IMem(  
    input [31:0] A,  
    output [31:0] RD);  
  
    parameter IMEM_SIZE=256;  
    reg [`DATA_WIDTH-1:0] RAM[IMEM_SIZE-1:0];  
    initial  
        $readmemh("C:/Users/nyodo/Desktop/cnt.txt",RAM);  
    assign RD=RAM[A];  
  
endmodule
```

```
module IF_ID(  
    input wire clk,rst,  
    input wire[31:0] In_pc,In_Ins,  
    input wire stall,clr,//branch_stall/clr determines whether it is a branch adventure  
    output reg[31:0] out_pc,out_Ins  
);  
    initial begin  
        out_pc = 32'b0;  
        out_Ins= 32'b0;
```


end

always@(posedge clk)begin

if(stall)begin

out_pc<=out_pc;

out_Ins<=out_Ins;

end

else if(clr) begin //clear val of pipeline reg for branch ins & next ins

out_pc<=32'b0;

out_Ins<=32'b0;

end

else begin

out_pc<=In_pc;

out_Ins<=In_Ins;

end

end

//Pipeline pause, pause PC and lock IF/ID registers

//pause for one clock cycle, lw is in mem stage,

//The next instruction remains in the ID/EX pipeline,

//decodes the value again, and the second instruction executes the IF operation again

Endmodule

module RegFile(CLK,WE3,RA1,RA2,WA3,WD3,RD1,RD2,RST);

parameter ADDR_SIZE=5;

input CLK,WE3;

input [ADDR_SIZE-1:0] RA1,RA2,WA3;

input [31:0] WD3;

output [31:0] RD1,RD2;

input RST;

//regfile

```

reg [31:0] rf[2**ADDR_SIZE-1:0];
//data in
integer i;
initial begin for(i=0;i<32;i=i+1) rf[i]<=32'b0; end
always @(posedge CLK,posedge RST) begin
    if(RST) for(i=0;i<2**ADDR_SIZE;i=i+1) rf[i]<=0;
    else if(WE3) rf[WA3]<=WD3;
end

//data rdout
assign RD1=(RA1!=0)?rf[RA1]:32'b0;
assign RD2=(RA2!=0)?rf[RA2]:32'b0;
endmodule

```

```

module Controller(
    input [5:0] Op,Funct,
    input Zero,
    output MemToReg,MemWrite,
    output Branch,ALUSrc,
    output RegDst,RegWrite,
    output Jump,
    output [2:0] ALUControl);

    wire [1:0] ALUOp;

    MainDec MainDec_1(Op,MemToReg,MemWrite,Branch,ALUSrc,RegDst,RegWrite,Jump,ALUOp);

    ALUDec ALUDec_1(Funct,ALUOp,ALUControl);

endmodule

```

```

module MainDec(
    input [5:0] Op,
    output MemToReg,MemWrite,
    output Branch,ALUSrc,
    output RegDst,RegWrite,
    output Jump,
    output [1:0] ALUOp);

```

```
reg [8:0] Controls;
```

```
assign {RegWrite,RegDst,ALUSrc,Branch,MemWrite,MemToReg,Jump,ALUOp}=Controls;
```

```
always @(*)
```

```
    case(Op)
```

```
        6'b000000: Controls <=9'b110000010;//R(ADD,SUB,or,xor,nor)TYPE
```

```
        6'b100011: Controls <=9'b101001000;//LW
```

```
        6'b101011: Controls <=9'b001010000;//SW
```

```
        6'b000100: Controls <=9'b000100001;//BEQ
```

```
        6'b001000: Controls <=9'b101000000;//ADDI
```

```
        6'b000010: Controls <=9'b000000100;//J
```

```
        default: Controls <=9'bxxxxxxx;//illegal Op
```

```
    endcase
```

```
endmodule
```

```
module ALUDec(
```

```
    input [5:0] Funct,
```

```
    input [1:0] ALUOp,
```

```
    output reg [2:0] ALUControl);
```

```
always @(*)
```

```
    case(ALUOp)
```

```
        2'b00:ALUControl <= 3'b010;// add for lw/sw/addi
```

```
        2'b01:ALUControl <= 3'b110;//sub for beq
```

```
        default: case(Funct)
```

```
            6'b100000: ALUControl <=3'b010; //add 2
```

```
            6'b100010: ALUControl <=3'b110; //sub 6
```

```
            6'b100100: ALUControl <=3'b000; //and 0
```

```
            6'b100101: ALUControl <=3'b001; //or 1
```

```
            6'b101010: ALUControl <=3'b111; //slt,cmp 7
```

```
            6'b100110: ALUControl <=3'b011; //xor 3
```

```
            6'b100111: ALUControl <=3'b100; //nor 4
```

```
            6'b000000: ALUControl <=3'b101; //sll 5
```

```
            default: ALUControl <=3'bxxx; //no idea
```

```
        endcase
```

```
    endcase
```

```
endmodule
```

```
module ID_EX(
```

```
    //input
```

```

input wire clk,clr,

input wire [31:0] RD1,RD2,ImmD,
input wire [4:0] rsD,rtD,rdD,
input wire RegWriteD, MemtoRegD, MemWriteD, ALUSrcD, RegDstD,
input wire [2:0] ALUControlD,
//output
output reg [31:0] RD1E,RD2E,ImmE,
output reg [4:0] rsE,rtE,rdE,
output reg RegWriteE, MemtoRegE, MemWriteE, ALUSrcE, RegDstE,
output reg [2:0] ALUControlE
);

initial begin
    RD1E<=32'b0;
    RD2E<=32'b0;
    ImmE<=32'b0;
    rsE<=5'b0;
    rtE<=5'b0;
    rdE<=5'b0;
    RegWriteE<=0;
    MemtoRegE<=0;
    MemWriteE<=0;
    ALUSrcE<=0;
    RegDstE<=0;
    ALUControlE<=3'b0;
end

always@(posedge clk) begin
    if(clr) begin
        RD1E<=32'b0;
        RD2E<=32'b0;
        ImmE<=32'b0;
        rsE<=5'b0;
        rtE<=5'b0;
        rdE<=5'b0;
        RegWriteE<=0;
        MemtoRegE<=0;
        MemWriteE<=0;
        ALUSrcE<=0;
        RegDstE<=0;
        ALUControlE<=3'b0;
    end
end

```

```

end
else begin
    RD1E<=RD1;
    RD2E<=RD2;
    ImmE<=ImmD;
    rsE<=rsD;
    rtE<=rtD;
    rdE<=rdD;
    RegWriteE<=RegWriteD;
    MemtoRegE<=MemtoRegD;
    MemWriteE<=MemWriteD;
    ALUSrcE<=ALUSrcD;
    RegDstE<=RegDstD;
    ALUControlE<=ALUControlD;
end
end
endmodule

```

```

module ALU_Forward(
    input[1:0]forwardAE,forwardBE,
    input ALUSrcE,
    input[31:0] ALUOutM,ResultW,RD1E,RD2E,SignImmE,

    output reg[31:0] SrcAE,SrcBE,WriteDataE
);
always@(*) begin
    case(forwardAE)
        2'b00:SrcAE<=RD1E;
        2'b01:SrcAE<=ResultW;
        2'b10:SrcAE<=ALUOutM;
    endcase

    case(forwardBE)
        2'b00:WriteDataE<=RD2E;
        2'b01:WriteDataE<=ResultW;
        2'b10:WriteDataE<=ALUOutM;
    endcase

    if(ALUSrcE)
        SrcBE<=SignImmE;
    end
end

```

```

    else
        SrcBE<=WriteDataE;
    end
end

```

```
endmodule
```

```
module ALU_8(F,CF,A,B,OP,OF,SF,PF,ZF);
```

```

    parameter SIZE=32;
    output reg [SIZE-1:0] F;
    output wire CF;
    input [SIZE-1:0] A,B;
    input [3:0] OP;
    output wire OF,SF,PF,ZF;
    parameter ALU_AND=4'b0000;//0
    parameter ALU_OR=4'b0001;//1
    parameter ALU_XOR=4'b0011;//3
    parameter ALU_NOR=4'b0100;//4
    parameter ALU_ADD=4'b0010;//2
    parameter ALU_SUB=4'b0110;//6
    parameter ALU_SLT=4'b0111;//7
    parameter ALU_SLL=4'b0101;//5

```

```

    wire [7:0] EN;
    wire [SIZE-1:0] FW;

```

```

always @(*) begin
    //ALU_AND: begin F<=FA;end
    //ALU_OR: begin F<=A|B;end
    //ALU_XOR: begin F<=A^B;end
    //ALU_NOR: begin F<=~(A|B);end
    F<=FW;
end

```

```

decoder38 decoder38_1(OP[2:0],EN);
NOR nor1(FW,A,B,EN[4]);
DIV div1(FW,A,B,EN[3]);
AND and1(FW,A,B,EN[0]);
OR or1(FW,A,B,EN[1]);
ADD add1(FW,CF,A,B,EN[2]);
SUB sub1(FW,CF,A,B,EN[6]);
CMP cmp1(FW,A,B,EN[7]);//slt

```

```

SLL sll1(FW,A,B,EN[5]);

assign ZF=(F==32'b0);//F==0
assign OF=A[SIZE-1]^B[SIZE-1]^F[SIZE-1]^CF;//overflow
assign SF=F[SIZE-1];//sign
assign PF=~^F;//odd or even of F's 1
endmodule

```

```

module NOR(FW,A,B,EN);
    parameter N=32;
    input [N-1:0] A,B;
    input EN;
    output reg [N-1:0] FW;

    always @(A,B,EN) begin
        if(EN==1) FW<=~(B|A);
        else FW<=32'bz;
    end
endmodule

```

*ALU 的各个操作例如上文 NOR 是由-, *, /等直接封装成模块实现的, 加法器、减法器、比较器是由二级进位先行加法器实现的, 实现代码在之前的实验 ALU Design 中已上传, 在此省略*

```

module EX_MEM(
    input wire[31:0] alu_output,WriteDataE,
    input wire[4:0] WriteRegE,
    input clk,rst,
    input wire RegWriteE,MemtoRegE,MemWriteE,

    output reg [31:0] ALUOutM,WriteDataM,
    output reg [4:0] WriteRegM,
    output reg RegWriteM,MemtoRegM,MemWriteM
);

    initial begin
        ALUOutM <= 32'b0;
        WriteDataM <= 32'b0;
        WriteRegM<=4'b0;
        RegWriteM<=1'b0;
        MemtoRegM<=1'b0;
        MemWriteM<=1'b0;
    end

    always@(posedge clk) begin

```

```

    ALUOutM <= alu_output;
    WriteDataM <= WriteDataE;
    WriteRegM <= WriteRegE;
    RegWriteM <= RegWriteE;
    MemtoRegM <= MemtoRegE;
    MemWriteM <= MemWriteE;

```

```

end

```

```

endmodule

```

```

module Dmemory(Data_out,clk,R_W,Addr,Data_in);
    output [31:0] Data_out;
    input clk;
    input R_W;
    input [31:0] Addr;
    input [31:0] Data_in;
    reg [31:0] data_memory[1023:0];
    integer i;
    initial begin
        for(i=0;i<1024;i=i+1) data_memory[i]=32'b0;
    end
    assign Data_out = R_W?32'b0:data_memory[Addr];

    always@(posedge clk) begin
        if(R_W)
            data_memory[Addr] <= Data_in;
    end
endmodule

```

```

module MEM_WB(
    //input
    input [31:0] ALUOutM,ReadDataM,
    input clk,rst,
    input [4:0] WriteRegM,
    input RegWriteM,MemtoRegM,

```



```

//output
output reg[31:0] ReadDataW,ALUOutW,
output reg[4:0] WriteRegW,
output reg RegWriteW,MemtoRegW
);

initial begin
    ALUOutW <= 32'b0;
    ReadDataW <= 32'b0;
    WriteRegW <= 5'b0;
    RegWriteW<=1'b0;
    MemtoRegW<=1'b0;
end

always@(posedge clk ) begin
    ALUOutW <= ALUOutM;
    ReadDataW <= ReadDataM;
    WriteRegW <= WriteRegM;
    RegWriteW <= RegWriteM;
    MemtoRegW <= MemtoRegM;

end

endmodule

module Hazard_unit(
    input [4:0] rsD,rtD,rsE,rtE,WriteRegE,WriteRegM,WriteRegW,
    input BranchD,MemtoRegE,RegWriteE,MemtoRegM,RegWriteM,RegWriteW,
    output reg stallF,stallD,flushE,
    output reg [1:0] forwardAE,forwardBE,forwardAD,forwardBD
);
    always @(*) begin//priority:M,W,E
        if ((rsE!=0) && (rsE==WriteRegM) && RegWriteM)
            forwardAE<=2'b10;
        else if ((rsE!=0) && (rsE==WriteRegW) && RegWriteW)
            forwardAE<=2'b01;
        else forwardAE<=2'b00;
    end

    always @(*) begin
        if ((rtE!=0) && (rtE==WriteRegM) && RegWriteM)
            forwardBE<=2'b10;
        else if ((rtE!=0) && (rtE==WriteRegW) && RegWriteW)

```


```


        forwardBE<=2'b01;
    else forwardBE<=2'b00;
end
wire lwstall,branchstall;
//handle decode data dependency for branch read regfile
//result in WB, alu ins MEM,OK
//result of alu ins in EX, lw in MEM, stall 1 cycle
always @(*)begin
    if((rsD!=5'b0)&&(rsD==WriteRegM)&&RegWriteM)
        forwardAD<=2'b01;
    else if((rsD!=5'b0)&&(rsD==WriteRegW)&&RegWriteW)
        forwardAD<=2'b10;
    else forwardAD<=2'b00;
end
always @(*)begin
    if((rtD!=5'b0)&&(rtD==WriteRegM)&&RegWriteM)
        forwardBD<=2'b01;
    else if((rtD!=5'b0)&&(rtD==WriteRegW)&&RegWriteW)
        forwardBD<=2'b10;
    else forwardBD<=2'b00;
end
//lw ins doesn't finish rd data til end of MEM stage
//e.g. lw produce $s0 at end of MEM but next and need $s0 at start EX(same cycle) ,STALL!
//load or branch stall
assign lwstall=((rsD==rtE)|| (rtD==rtE))&&MemtoRegE;
assign branchstall=(BranchD && RegWriteE && (WriteRegE==rsD || WriteRegE==rtD) )||
                    (BranchD && MemtoRegM && (WriteRegM==rsD || WriteRegM==rtD) );
always @(*)begin


    {stallF,stallD,flushE}<={lwstall||branchstall,lwstall||branchstall,lwstall||branchstall};
end
endmodule


```

实验代码的仿真电路图:

 

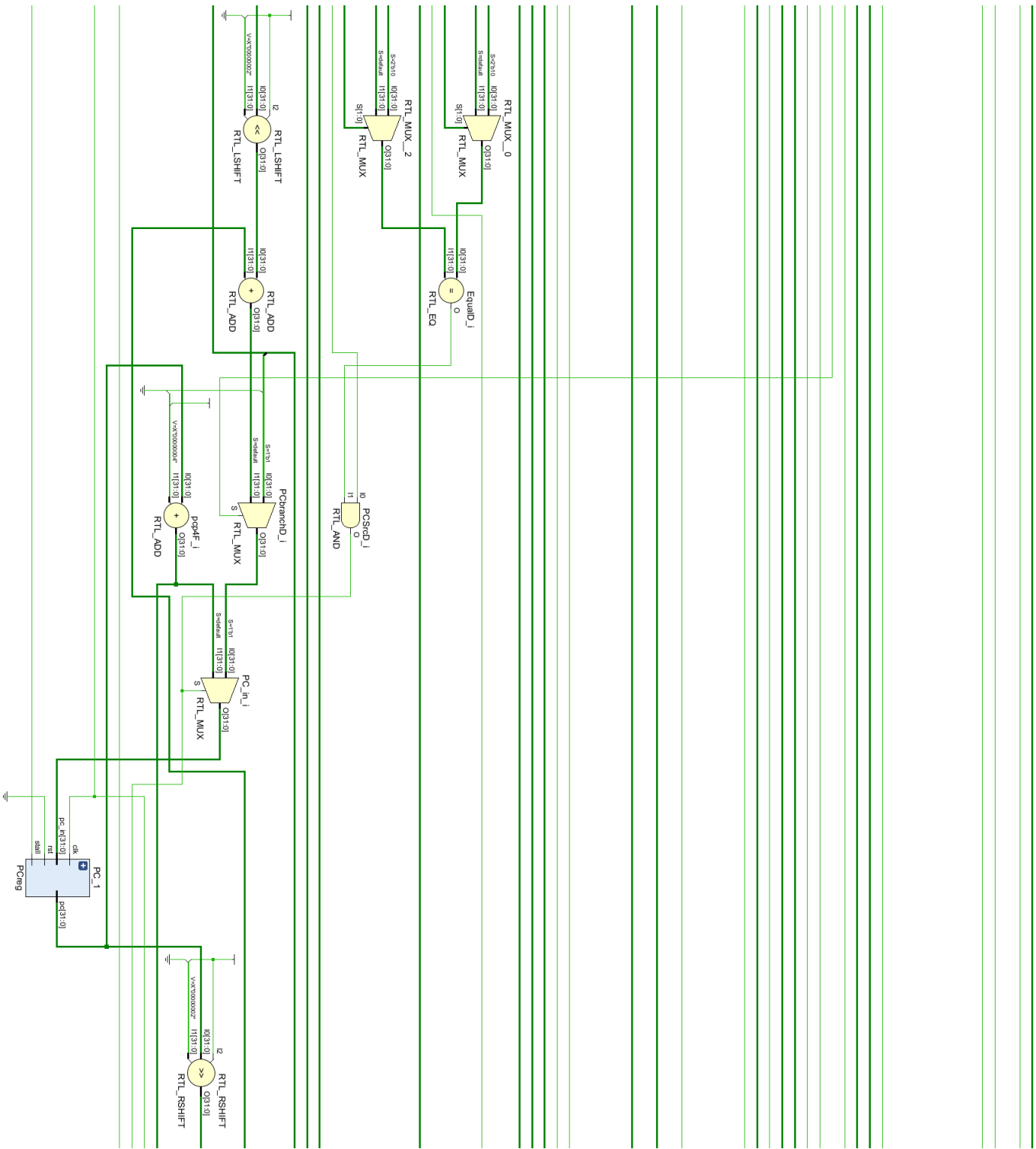

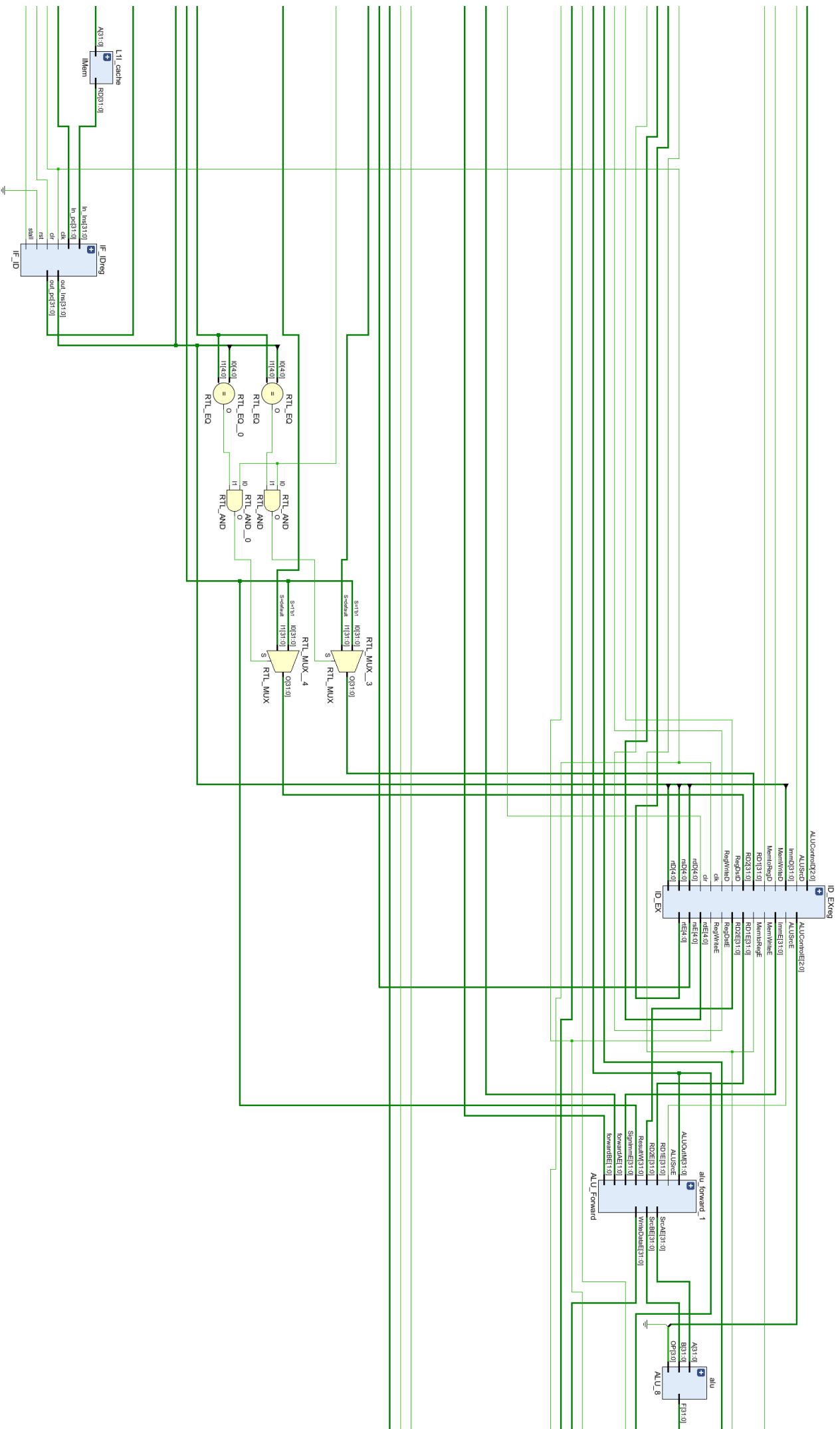

 

所有部件均在上图正确连线

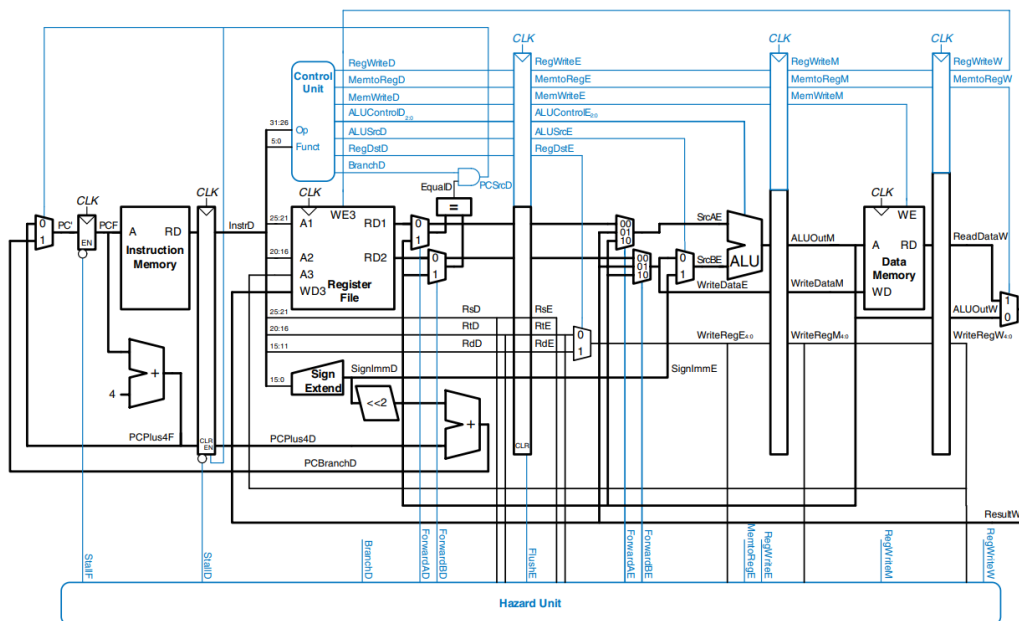


Figure 7.58 Pipelined processor with full hazard handling

本流水线处理器在上图的改动是：

将 $PCSrcD = (BranchD | JumpD) \& EqualD$; , 判断多增加一个 jump 选项, 由于 jump 指令使用 $imm[15:0]$ 跳转, 所以此时 $equalD$ 一定是 1, 满足 $PCSrcD=1$, 在 Hazard_unit 中, 入口 $BranchD = ControlUnit$ 里面的 $BranchD | JumpD$

所有级寄存器实现是简单的存贮与读取, 而存储、逻辑、运算单元与单周期 CPU 基本一致。主要是 Hazard_Unit 单元的设计

首先涉及到的是数据的转发,

对于 Branch, 如果判断数据 WB 阶段, 前半周期就会写到寄存器, 后半周期读取, 没有冒险存在, 但是在 ID 阶段收到 MEM 的数据转发, 用于判断 $EqualD$ 。如果判断数据在 EX 阶段, 或者是 lw 的结果, 那么流水线必须停顿至数据准备完成。

所以判断逻辑为:

$ForwardAD = (rsD \neq 0) \text{ AND } (rsD == WriteRegM) \text{ AND } RegWriteM$

$ForwardBD = (rtD \neq 0) \text{ AND } (rtD == WriteRegM) \text{ AND } RegWriteM$

说明 branch 的 rs, rd 与 MEM 阶段的 rs, rd 地址相同

$lwstall = ((rsD == rtE) || (rtD == rtE)) \& \& MemtoRegE$

如果 ID 与 EX 操作数的调用有重叠且 EX 准备向 reg 中写入 (说明是 lw), 有 RAW 冒险, 必须要停顿 1 cycle,

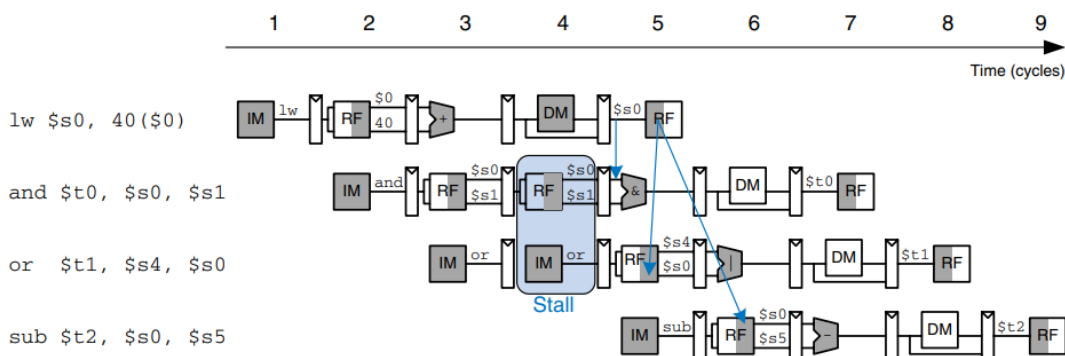


Figure 7.52 Abstract pipeline diagram illustrating stall to solve hazards

对于 branch lw 连续使用, 则会停顿两个周期

$\text{branchstall} = \text{BranchD} \text{ AND } \text{RegWriteE} \text{ AND } (\text{WriteRegE} == \text{rsD} \text{ OR } \text{WriteRegE} == \text{rtD})$

OR

$\text{BranchD} \text{ AND } \text{MemtoRegM} \text{ AND } (\text{WriteRegM} == \text{rsD} \text{ OR } \text{WriteRegM} == \text{rtD})$

如果 ID 是 branch, EX 阶段有向 branch 的 rs, rd 写入操作或者 lw 在 MEM 阶段准备写入 rs, rd 则 branch stall,

$\text{StallF} = \text{StallD} = \text{FlushE} = \text{lwstall} \text{ OR } \text{branchstall}$

IF/ID 寄存器与 PC 取指必须停顿, ID/EX 清空为 nop 气泡

对于 ALU 运算, 如果所需操作数在 MEM, WB 阶段, 必须进行转发

所以这里的多路选择器判断逻辑为

以下为 forwardBE 判断逻辑, forwardAE 与之相同, rt 变为 rs 即可

```
if ((rtE!=0) && (rtE==WriteRegM) && RegWriteM)
    forwardBE<=2'b10;
else if ((rtE!=0) && (rtE==WriteRegW) && RegWriteW)
    forwardBE<=2'b01;
else forwardBE<=2'b00;
```

即最先选择 MEM 的转发,

之后选择 WB 的转发, 最后选择当前读出来的寄存器数, 是有优先级的考虑的

还有一个改动逻辑是

ID/EX 寄存器读入寄存器的转发,

如下代码为例

```
addi $3,$2,20
```

```
sw $3,3
```

```
addi $4,$2,4
```

```
add $4,$2,$3
```

由于 ID/EX 寄存器读入的时机为周期前半段, 上段代码 \$3 在时钟末期写入寄存器, 所以必须要将 ResultW 提前半个周期转发给 ID/EX 读入口, 逻辑为:

```
.RD1((RegWriteW&&rs==WriteRegW)?ResultW:SrcA),
.RD2((RegWriteW&&rt==WriteRegW)?ResultW:SrcB),
```

课本中的理想化的寄存器堆采用前半周期写后半周期读, 所以不存在这种数据冒险。

实际实现中, 寄存器堆在 WB 级的结束时才写入值, 所以对于 **lw 后跟 branch** 指令在 **lw 的 WB 周期** 读取的寄存器的值是旧值, 存在数据冒险在 id 级产生两个旁路信号, 选择正确的数据源

逻辑为:

```
if((rsD!=5'b0)&&(rsD==WriteRegM)&&RegWriteM)
    forwardAD<=2'b01;
else if((rsD!=5'b0)&&(rsD==WriteRegW)&&RegWriteW)
    forwardAD<=2'b10;
else forwardAD<=2'b00;
```


基础功能测试:

```
main:
addi $2,$2,10
sw $2,2
addi $3,$2,20
sw $3,3
addi $4,$2,4
add $4,$2,$3
sw $4, 4
addi $0,$4,44
lw $4,4($2)
sw $0,8($2)
sub $2,$4,$3
and $1,$2,$4
or $5,$6,$2
sub $7,$2,$8
or $2,$4,$3
and $2,$4,$3
slt $2,$4,$3
lw $0,40($0)
and $1,$0,$2
or $3,$4,$0
sub $5,$0,$6
or $3,$4,$0
beq $3,$3,equ
lw $2,0($3)
equ:
beq $3,$4,exit
or $2,$4,$3
and $2,$4,$3
slt $2,$4,$3
sw $2,0($3)
exit:
j main
```

以上为一段包含所有指令的循环代码,

翻译为机器码为

2042000a

ac020002


20430014

ac030003

20440004

00432020
ac040004
2080002c
8c440004
ac400008
00831022
00440824
00c22825
00483822
00831025
00831024
0083102a
8c000028
00020824
00801825
00062822
00801825
10630001
8c620000
10640004
00831025
00831024
0083102a
ac620000
08000000

Address	Code	Basic	
0x00000000	0x2042000a	addi \$2,\$2,10	2: addi \$2,\$2,10
0x00000004	0xac020002	sw \$2,2(\$0)	3: sw \$2,2
0x00000008	0x20430014	addi \$3,\$2,20	4: addi \$3,\$2,20
0x0000000c	0xac030003	sw \$3,3(\$0)	5: sw \$3,3
0x00000010	0x20440004	addi \$4,\$2,4	6: addi \$4,\$2,4
0x00000014	0x00432020	add \$4,\$2,\$3	7: add \$4,\$2,\$3
0x00000018	0xac040004	sw \$4,4(\$0)	8: sw \$4,4
0x0000001c	0x2080002c	addi \$0,\$4,44	9: addi \$0,\$4,44
0x00000020	0x8c440004	lw \$4,4(\$2)	10: lw \$4,4(\$2)
0x00000024	0xac400008	sw \$0,8(\$2)	11: sw \$0,8(\$2)
0x00000028	0x00831022	sub \$2,\$4,\$3	12: sub \$2,\$4,\$3
0x0000002c	0x00440824	and \$1,\$2,\$4	13: and \$1,\$2,\$4
0x00000030	0x00c22825	or \$5,\$6,\$2	14: or \$5,\$6,\$2
0x00000034	0x00483822	sub \$7,\$2,\$8	15: sub \$7,\$2,\$8
0x00000038	0x00831025	or \$2,\$4,\$3	16: or \$2,\$4,\$3
0x0000003c	0x00831024	and \$2,\$4,\$3	17: and \$2,\$4,\$3
0x00000040	0x0083102a	slt \$2,\$4,\$3	18: slt \$2,\$4,\$3
0x00000044	0x8c000028	lw \$0,40(\$0)	19: lw \$0,40(\$0)
0x00000048	0x00020824	and \$1,\$0,\$2	20: and \$1,\$0,\$2
0x0000004c	0x00801825	or \$3,\$4,\$0	21: or \$3,\$4,\$0
0x00000050	0x00062822	sub \$5,\$0,\$6	22: sub \$5,\$0,\$6
0x00000054	0x00801825	or \$3,\$4,\$0	23: or \$3,\$4,\$0
0x00000058	0x10630001	beq \$3,\$3,1	24: beq \$3,\$3,eq
0x0000005c	0x8c620000	lw \$2,0(\$3)	25: lw \$2,0(\$3)
0x00000060	0x10640004	beq \$3,\$4,4	27: beq \$3,\$4,exit
0x00000064	0x00831025	or \$2,\$4,\$3	28: or \$2,\$4,\$3
0x00000068	0x00831024	and \$2,\$4,\$3	29: and \$2,\$4,\$3
0x0000006c	0x0083102a	slt \$2,\$4,\$3	30: slt \$2,\$4,\$3
0x00000070	0xac620000	sw \$2,0(\$3)	31: sw \$2,0(\$3)
0x00000074	0x08000000	j 0x00000000	33: j main

 

第一个是 addi 指令，在第二周期可以看到 rs=2, rt=2, 第三周期看到 immE=0xa, SrcBE=0xa, aluoutputE 所得为 0xa, 说明流水线工作正常，i 型指令正常

第二个是 sw \$t0, 2(\$t0)，可以看到第三周期 rs=0, rt=2, imm=2, 第四周期 writeDataE=0xa, 说明把刚才的 addi 的值存进了 Dmem 中

0xac400008 至 0x0083102a 均为 R 型指令
从解码、读取，运算的值来看都是正常的

0x8c000028 是 lw 指令


lw \$0, 40(\$0)

and \$1, \$0, \$2

or \$3, \$4, \$0

sub \$5, \$0, \$6

这一段拥有 RAW 冒险，以及需要各种阶段的转发

 


我们可以看到，在 0x0080125 的时候触发了 stall，此时 EX 阶段的 alu_result 是 0x28，正是 40(\$0)，它即将作为 Dmem 的 addr，可以看到，在停顿的第二周期，ID/EX 寄存器的内容全部被清零，例如 rsE, rtE, AluSrcE, MemtoRegE 等信号都是 0，它不与上一周期的 lw 的 ID/EX 寄存器值相同，再下一个周期，才开始解码 or 指令

从前面的代码我们知道，lw 指令前\$0 值为 44(0x2c)，这个可以从图中第十周期 lw 的 AluResultE 看出，那么在 lw 后调用的 add, or, sub 都是 lw 后加载的新值 (\$0) = 0, 说明 RAW 问题已经得到解决，数据的转发也是没有问题的。

之后是一段跳转指令

```
beq $3,$3, equ
lw $2, 0($3)
equ:
beq $3,$4, exit
or $2,$4,$3
and $2,$4,$3
slt $2,$4,$3
sw $2, 0($3)
exit:
j main
```

 beq \$3,\$3,eq 的机器码为 0x10630001, 可以看到, 在下一周期 beq 的 ID 阶段流水线停顿, 这是因为 beq 用到的\$3 是上一个指令 or 的结果, 此次指令分支要跳到 eq 处, 即 10640001, 而且, 我们可以看到, lw 的 rs=3, rt=2, 然而在解码阶段没有 rs=3, rt=2 出现, 仅仅是 beq \$3,\$3,eq 的 rs=3, rt=3 后, IF/ID 寄存器被刷新, 紧接着是 beq \$3,\$4,exit 解码出来的 rs=3, rt=4, lw 仅仅存在在 IF 阶段后就被清除了

0x8c620000 有一次停顿, 其实这是因为 branch 要用到 or 的操作结果\$3 所以停顿的。\$3 停顿的时候值为 0x1e, 停顿后的值为 0x0

eq 函数中, (\$3)==(\$4)=0,

所以仅在 IF 阶段读取了 or \$2,\$4,\$3 指令后至今 branch 到 exit 函数, pc_in 从

0x64 变到 0x74。下一个周期, IF 取指为 0x08000000, jump 到第一条指令, 可以看到, 此时 IF 指令停顿 2 个周期, 这是因为 jump 指令到 ID 阶段后指令空了, IF 取不到正确的指令了, 然后 jump 又在 ID 阶段暂停一个周期, 这是因为我把 jump 和 branch 的冒险信号做到了一起, 理论上分开的话是不用停顿一个周期的, 所以两个周期后, PC 重新变为 0x0, 开始新一轮循环, 整个流程是正确的。

将测试代码换为如下：

```
main:
addi $2,$2,10
sw $2,34
addi $3,$2,20
addi $1,$2,20
sw $3,3
addi $4,$2,4
add $4,$2,$3
sw $4, 4
addi $0,$4,44
lw $3,4($3)
beq $3,$1,eq
and $1,$0,$2
or $3,$4,$0
sub $5,$0,$6
or $3,$4,$0
beq $3,$3,eq
lw $2,0($3)
eq:
beq $3,$4,exit
or $2,$4,$3
and $2,$4,$3
slt $2,$4,$3
sw $2,0($3)
exit:
j main
```


主要关注这两句，这里

```
lw $3,4($3)
```

```
beq $3,$1,eq
```

beq 要使用 lw 的值，


	0x00000020	0x2080002c	addi \$0,\$4,44	10: addi \$0,\$4,44
	0x00000024	0x8c630004	lw \$3,4(\$3)	11: lw \$3,4(\$3)
	0x00000028	0x10610006	beq \$3,\$1,6	12: beq \$3,\$1,eq
	0x0000002c	0x00020824	and \$1,\$0,\$2	13: and \$1,\$0,\$2
	0x00000030	0x00801825	or \$3,\$4,\$0	14: or \$3,\$4,\$0
	0x00000034	0x00062822	sub \$5,\$0,\$6	15: sub \$5,\$0,\$6
	0x00000038	0x00801825	or \$3,\$4,\$0	16: or \$3,\$4,\$0
	0x0000003c	0x10630001	beq \$3,\$3,1	17: beq \$3,\$3,eq
	0x00000040	0x8c620000	lw \$2,0(\$3)	18: lw \$2,0(\$3)
	0x00000044	0x10640004	beq \$3,\$4,4	20: beq \$3,\$4,exit

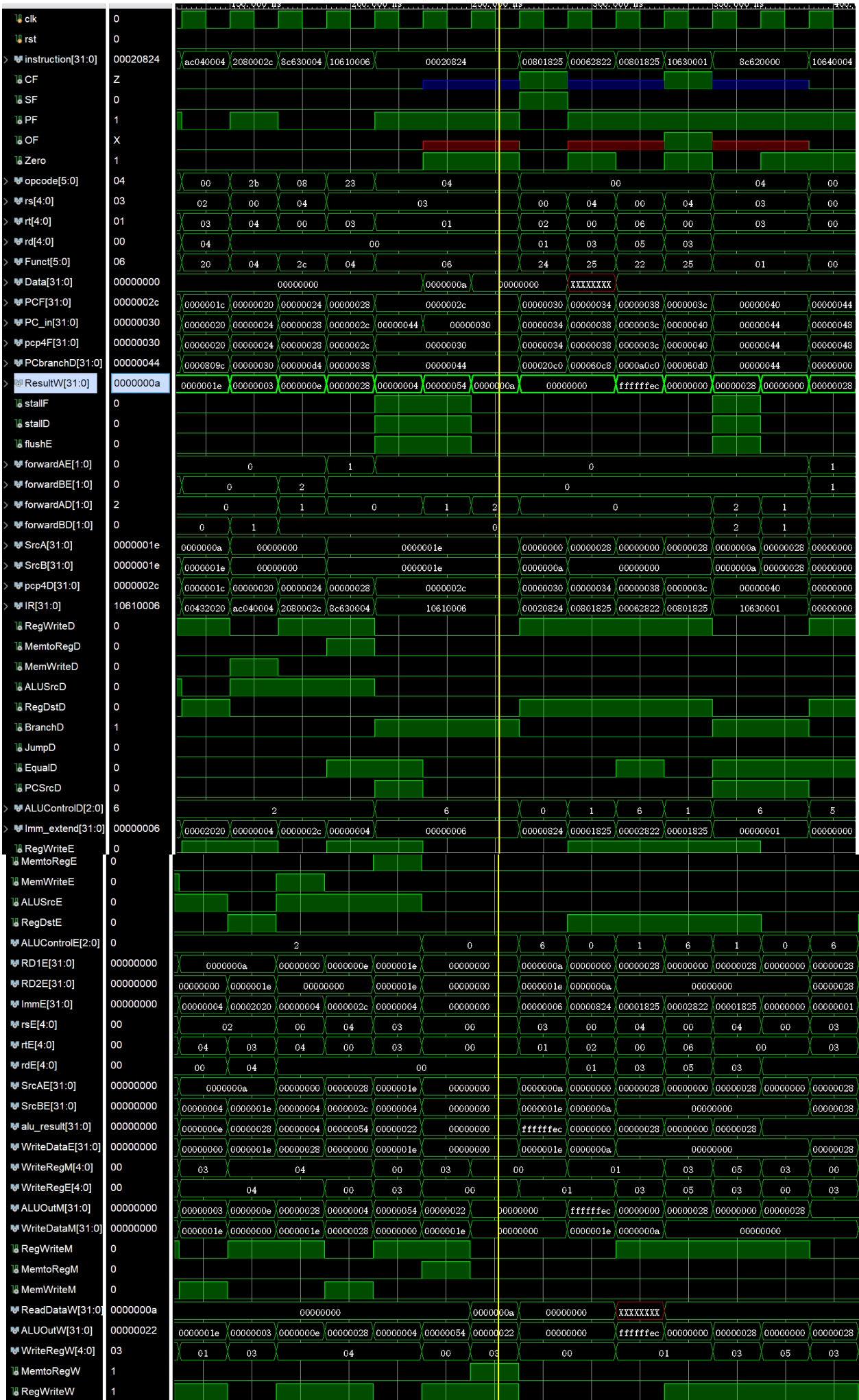

仿真如下：

0x8c630004 是 1w 指令, 1w 在 EX 阶段时候 beq 在 ID 阶段, 由于 beq 需要 1w 的 \$3, 所以至少要 1w 在 EX 阶段末才能得到 \$3, 于是流水线停顿一次, 1w 在 MEM 阶段时, 可以看到 aluoutM 是 0x22, 正是 4(\$3) 的值, 作为 Dmem 的读取地址, 此时是停顿的第二个周期, 由于 branchstall 里面 MEM 阶段有 ID 要用的操作数, 所以 branchstall 又停顿一个周期, 直到 1w 进入 WB 阶段, 此时寄存器还没有将 \$3 的值更新, 所以要将 resultW 也就是 (\$3)=0xa 前递到 branch 的 EqualD 的计算中, 而此时 (\$1)=SrcB=0x1e, 两者不相等, 所以 PC_in 没有变成 PCbranchD, 而是普通 +4.

如果将\$3 的值保持为 0x1e，更改上述代码，重新观察得

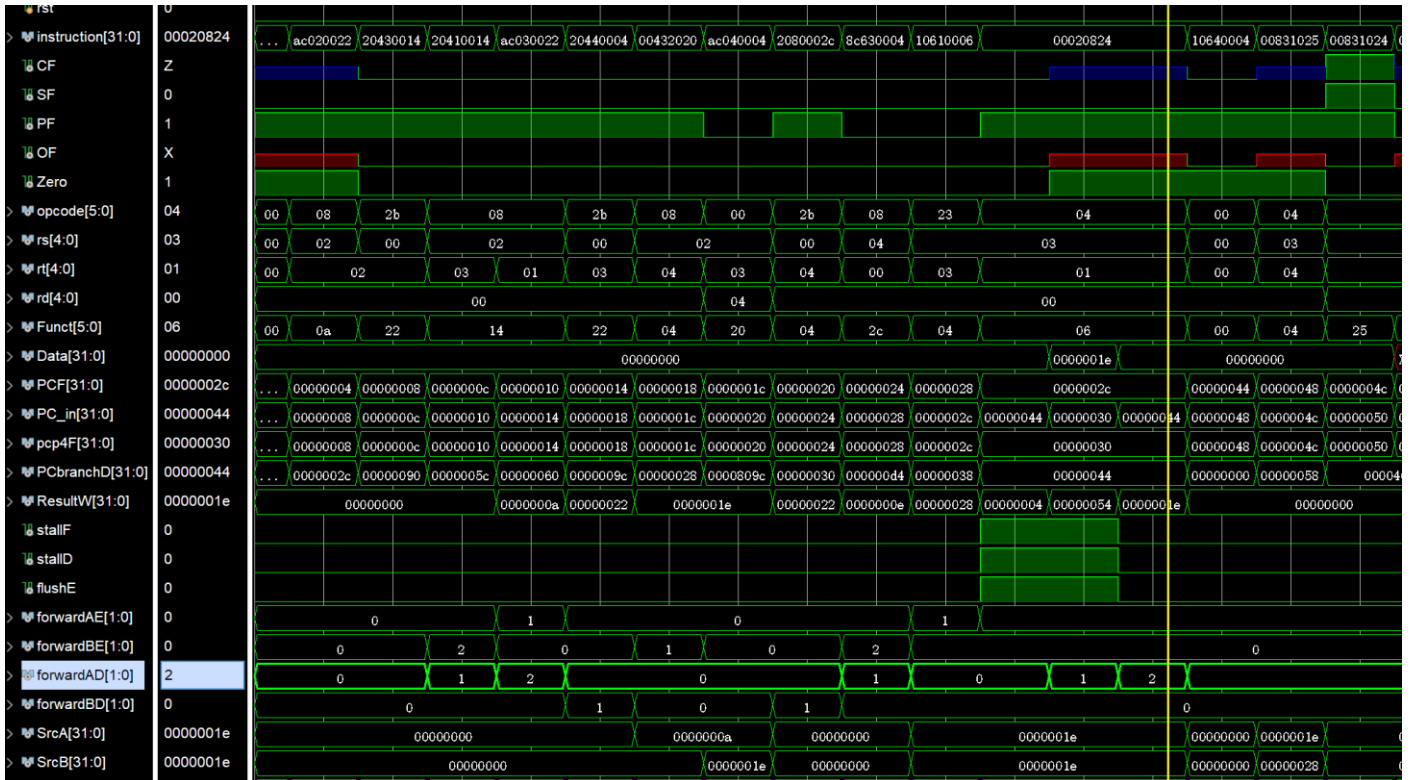

可以看到此时便成功地跳到了 PC=0x44 处，说明 lw 和 branch 这种最极端的冒险情况也是正常运行的

五、调试和心得体会

设计流水线 CPU 是一个浩大的工程,除了按图说话设计出整体数据通路外,最主要的是考虑到所有的冒险行为,从普通的 WB/MEM→EX 转发到 branch 和 lw 的停顿与 WB→ID 转发的结合,各个地方都要细致考虑,CPU 设计是一个宏观又极为精细的活。这次实验使我大大增强了对 CPU 基本运行逻辑的理解,也对整个工程设计的思路,从宏观到细节的把握能力有了很大的锻炼,非常有意义。